

6.2.1: Electromotive Force and Internal Resistance

The reader is reminded of the following definition from section 4.1:

Definition. The potential difference across the poles of a cell when no current is being taken from it is called the *electromotive force* (EMF) of the cell.

I shall use the symbol E for EMF.

Question. A $4\ \Omega$ resistance is connected across a cell of EMF 2 V. What current flows?

The immediate answer is 0.5 A – but this is likely to be wrong. The reason is that a cell has a resistance of its own – its *internal resistance*. The internal resistance of a lead-acid cell is typically quite small, but most dry cells have an appreciable internal resistance. If the external resistance is R and the internal resistance is r , the total resistance of the circuit is $R + r$, so that the current that flows is $E/(R + r)$.

Whenever a current is taken from a cell (or battery) the potential difference across its poles *drops* to a value less than its EMF. We can think of a cell as an EMF in series with an internal resistance:

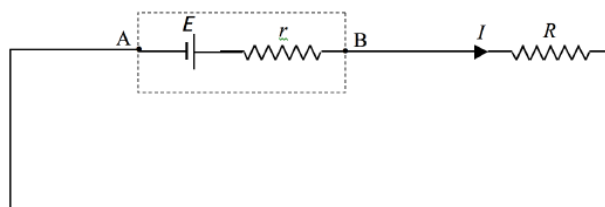


FIGURE IV.4

If we take the point A as having zero potential, we see that the potential of the point B will be $E - Ir$, and this, then, is the potential difference across the poles of the cell when a current I is being taken from it.

? Show that this can also be written as $\frac{ER}{R+r}$.

This page titled [6.2.1: Electromotive Force and Internal Resistance](#) is shared under a [CC BY-NC 4.0](#) license and was authored, remixed, and/or curated by [Jeremy Tatum](#) via [source content](#) that was edited to the style and standards of the LibreTexts platform.