

## CHAPTER OVERVIEW

### 20: Circuits and Direct Currents

**Topic hierarchy**

- 20.1: Overview
- 20.2: Resistors in Series and Parallel
- 20.3: Kirchhoff's Rules
- 20.4: Voltmeters and Ammeters
- 20.5: RC Circuits

---

This page titled [20: Circuits and Direct Currents](#) is shared under a [not declared](#) license and was authored, remixed, and/or curated by [Boundless](#).