

CHAPTER OVERVIEW

3: Direct Current Circuits

[3.1: Moving Charge](#)

[3.2: Resistance and Energy Dissipation](#)

[3.3: Networks of Batteries and Resistors](#)

[3.4: Kirchhoff's Rules](#)

[3.5: RC Circuits](#)

This page titled [3: Direct Current Circuits](#) is shared under a [CC BY-SA 4.0](#) license and was authored, remixed, and/or curated by [Tom Weideman](#) directly on the LibreTexts platform.