

5.6: Circuit Problem Solving

Solving Electric Circuit Problems

When tackling a circuit problem you may need to figure out the equivalent resistance of the circuit, voltage drops across resistors, total current coming out of the battery or current through specific resistors, power dissipated by resistors or provided by the battery, relative brightness of light bulbs in a circuit, the effect of a shorted resistor, or a burnt one, and more.

Below are a few useful steps to follow. Even though these basics steps are provided, it is never a good idea to follow a procedure verbatim. This procedure is a good starting guide of tackling some circuit problems, but might not apply to all of them in the order provided. As you start working with more advanced scenarios, think of ways of how you can work backwards, follow the steps in different order, or only use some of the steps to solve your particular problem most efficiently.

Circuit problem solving procedure:

1) Calculate the **equivalent resistance** of the circuit. First combine all the series resistors and then calculate the parallel ones. Use the following equations:

$$\text{series : } R_{eq} = \sum_i^n R_i \quad (5.6.1)$$

$$\text{parallel : } \frac{1}{R_{eq}} = \sum_i^n \frac{1}{R_i} \quad (5.6.2)$$

2) Use your result of equivalent resistance to find the **total current** coming out of the battery:

$$I_{tot} = \frac{\mathcal{E}}{R_{eq}} \quad (5.6.3)$$

3) Apply the **loop rule** to all the loops present in the circuit in order to find the relationship between voltage drops and emf of battery. Make sure you are consistent with the direction of the loop you choose. If your loop takes you from a negative to the positive terminal of the battery, you will get, $+\mathcal{E}$. If you loop takes you across a resistor in the direction of the current, then the correct sign of the voltage difference should be negative, $\Delta V = -IR$. In general for any given loop, the following must be true:


$$\sum \mathcal{E} + \sum \Delta V = 0 \quad (5.6.4)$$

4) Apply the **junction rule** at all the junctions to find the relationship between the current going into the junction and the individual currents in each of n paths:

$$I_{in} = \sum_i^n I_i \quad (5.6.5)$$

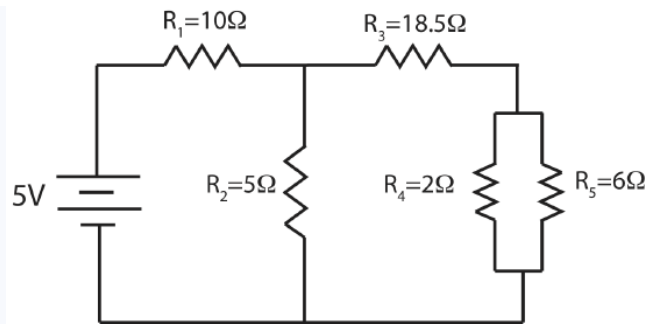
Example 5.6.1

For the circuit show below find the current and voltage for each of the five resistors.



Solution

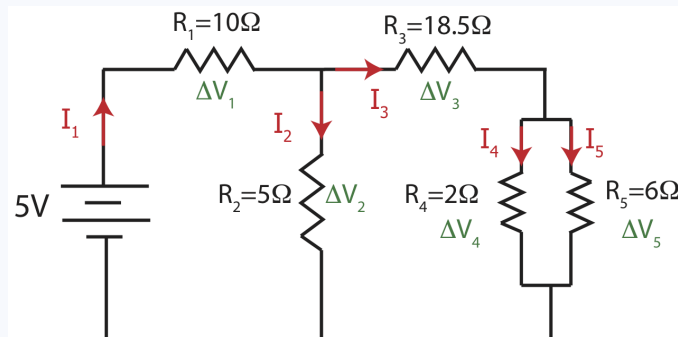It is a good idea to start by labeling all the currents and voltage as shown below.



Since all the resistances are known, the first natural step is to find the equivalent resistance. For this particular circuit the best way to combine resistors is: resistors 4 and 5 are in parallel, their combination R_{45} is in series with R_3 . The combination of 3, 4, and 5, R_{345} is in parallel with 2, and their combination, R_{2345} is in series with R_1 .

First, calculating R_4 and R_5 in parallel:

$$\frac{1}{R_{45}} = \frac{1}{R_4} + \frac{1}{R_5} = \frac{1}{2\Omega} + \frac{1}{6\Omega} = \frac{2}{3\Omega}$$

$$R_{45} = \frac{3}{2}\Omega$$

Combining R_3 in series with R_{45} :

$$R_{345} = R_3 + R_{45} = 18.5\Omega + 1.5\Omega = 20\Omega$$

Combining R_3 in parallel with R_{345} :

$$\frac{1}{R_{2345}} = \frac{1}{R_2} + \frac{1}{R_{345}} = \frac{1}{5\Omega} + \frac{1}{20\Omega} = \frac{1}{4\Omega}$$

$$R_{2345} = 4\Omega$$

And finally combining R_1 in series with R_{2345} to find the equivalent resistance of this circuit:

$$R_{eq} = R_1 + R_{2345} = 10\Omega + 4\Omega = 14\Omega$$

Resistor 1 is the only resistors which is in series with the battery, so the current through resistor 1, I_1 , will be equal to the total current coming out of the battery:

$$I_1 = I_{tot} = \frac{\mathcal{E}}{R_{eq}} = \frac{5V}{14\Omega} = 0.357A$$

Once we know the current through 1, we can find the voltage across resistor 1:

$$\Delta V_1 = -I_1 R_1 = 0.357A \times 10\Omega = -3.57V$$

Now we can apply the loop rule to the first loop on the left that goes through the battery, resistor 1, and resistor 2 to find the voltage across resistor 2:

$$\mathcal{E} + \Delta V_1 + \Delta V_2 = 0$$

$$\Delta V_2 = -\mathcal{E} - \Delta V_1 = -5V + 3.57V = -1.43V$$

Since we know the voltage across resistors 2, we can figure out the current through that resistor, I_2 :

$$I_2 = \frac{-\Delta V_2}{R_2} = \frac{1.43V}{5\Omega} = 0.286A$$

Next, we can use the junction rule to find the amount of current that goes to the other branch and through resistors 3, I_3 :

$$I_1 = I_2 + I_3$$

$$I_3 = I_1 - I_2 = 0.357A - 0.286A = 0.071A$$

Knowing the current, allows us to find the voltage drop across R_3 :

$$\Delta V_3 = -I_3 R_3 = -0.071A \times 18.5\Omega = -1.3135V$$

Applying the loop rule to the outermost loop we can find the voltage drop across the parallel combination of R_4 and R_5 :

$$\mathcal{E} + \Delta V_1 + \Delta V_3 + \Delta V_{45} = 0$$

$$\Delta V_{45} = -\mathcal{E} - \Delta V_1 - \Delta V_3 = -5V + 3.57V + 1.3135V = -0.1165V$$

Lastly, since we know the voltage drop across the parallel set of 4 and 5, it must equal to the voltage drops across each one of the resistors, $\Delta V_{45} = \Delta V_4 = \Delta V_5$. Using this, we can find the currents I_4 and I_5 :

$$I_4 = \frac{-\Delta V_4}{R_4} = \frac{0.1165V}{2\Omega} = 0.0583A$$

$$I_5 = \frac{-\Delta V_5}{R_5} = \frac{0.1165V}{6\Omega} = 0.0194A$$

Example 5.6.2


While playing with electronics in class you build a circuit with one battery and five resistors. You calculate the following equivalent resistance:

$$R_{eq} = \left[\frac{1}{R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}} + \frac{1}{R_4} \right]^{-1} + R_5$$

- Draw a possible circuit connected to a battery that has the above equivalent resistance. Clearly mark each resistor with R_1 , R_2 , R_3 , R_4 , and R_5 .
- Assume that $R_{eq} = 25\Omega$, $R_4 = R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$, and $R_2 = 2R_3$. If the circuit is connected to a 10V battery, how much current will flow through R_2 ?
- If R_2 was shorted out, what would be the new equivalent resistance in terms of the resistor numbers? Would the total current coming out of the battery increase, decrease, or stay the same?

Solution

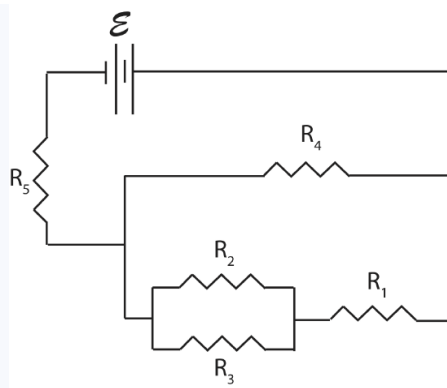a) The equation above states that R_5 is in series with a parallel branch which contains R_4 in one path and $R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$ in the other. The other path has R_1 in series with a parallel branch containing R_2 and R_3 as shown.



b) The total current coming out of the battery is

$$I = \frac{\mathcal{E}}{R_{eq}} = \frac{10V}{25\Omega} = 0.4A$$

The two paths of the main parallel branch have equal resistance, so the current will split equally at the junction. This means that half the total current will flow through R_1 , which is $0.2A$. The current will split further between R_2 and R_3 . Since $R_2 = 2R_3$, R_3 will get double the current of R_2 since their voltage drops have to be the same.

$$\Delta V_2 = \Delta V_3$$

$$I_2 R_3 = I_3 R_3$$

$$I_2 = \frac{I_3}{2}$$

Using the fact that $I_2 + I_3 = 0.2A$ and the above result we get:

$$I_2 = \frac{I_3}{2} = \frac{0.2 - I_2}{2}$$

Resulting in $I_2 = \frac{1}{15} A$.


c) If R_2 was shorted out, all the current going through R_1 would go through the wire, so R_2 and R_3 would not get any current and are no longer part of the active circuit. The new equivalent resistance becomes:

$$R_{eq} = R_5 + \left(\frac{1}{R_4} + \frac{1}{R_1} \right)^{-1}$$

Since the lower branch now has reduced resistance, the combined resistance between R_4 and the lower branch will decrease, thus the total equivalent resistance of the entire circuit will be decreased. Smaller total resistance means that the total current will increase since, $I = \frac{\mathcal{E}}{R_{eq}}$.

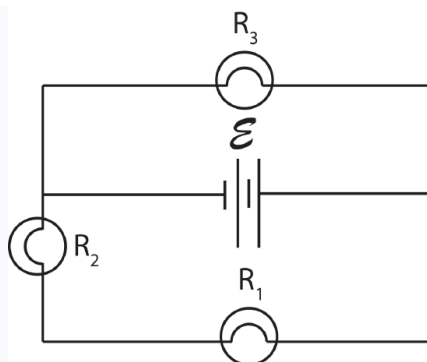Example 5.6.3

You build the circuit shown here and find that the brightness of light bulb 1 is twice as bright (double power) as 3, and the brightness of light bulb 1 is half as bright as 2 (half power).



- You know that light bulb 3 has resistance of 36Ω . Find the resistance of light bulbs 1 and 2.
- You add a wire across light bulb 1. Describe what happens to the brightness of each light bulb (gets brighter, gets dimmer, stays the same brightness, or is not lit) compared to the original circuit.
- If light bulb 1 in the original circuit burnt out instead, what happens to the brightness of each light bulb (gets brighter, gets dimmer, stays the same brightness, or is not lit) compared to the original circuit?

Solution

a) Resistors R_1 and R_2 have the same current since they are in series, $I_1 = I_2$. Since $P = I^2 R$ and $P_2 = 2P_1$ we conclude that:

$$P_2 = I^2 R_2 = 2P_1 = 2I^2 R_1$$

$$R_2 = 2R_1$$

When it comes to resistors in parallel, it is often simpler to think in terms of voltage drops rather than current. The voltage drop across R_3 has to equal to the voltage drop across the other branch which includes the sum of voltage drop across R_1 and R_2 :

$$\Delta V_3 = \Delta V_1 + \Delta V_2$$

Since $R_2 = 2R_1$ and $\Delta V = -IR$, $\Delta V_2 = 2\Delta V_1$, and the above equation becomes:

$$\Delta V_3 = 3\Delta V_1$$

We also know that $P_1 = 2P_3$. Using $P = \frac{\Delta V^2}{R}$ we find that:

$$\frac{\Delta V_1^2}{R_1} = 2 \frac{\Delta V_3^2}{R_3}$$

Using the result $\Delta V_3 = 3\Delta V_1$ we find that:

$$\frac{\Delta V_1^2}{R_1} = 18 \frac{\Delta V_1^2}{R_3}$$

$$R_3 = 18R_1$$

Using $R_3 = 36\Omega$, we find that $R_1 = 2\Omega$, and using $R_2 = 2R_1$, we find that $R_2 = 4\Omega$.

b) Adding a wire across R_1 shorts out R_1 , since all the current will go through the wire. So R_1 will not be lit. The voltage drop across R_2 has to increase, since due to the loop rule applied to the bottom loop, all the voltage now drops across rather R_2 , $\mathcal{E} = -\Delta V_2$, rather than being split between R_1 and R_2 in the original circuit. Since power is proportional to voltage drop, 2 gets brighter. The voltage drop across R_3 doesn't change due to loop rule for top loop, $\mathcal{E} = -\Delta V_3$, so 3 stays the same brightness.

c) If light bulb 1 burns out, the path on the lower loop is broken (there is no place for current to go), so both R_1 and R_2 will not be lit. The voltage drop across R_3 doesn't change due to loop rule for top loop as in the argument for b), so 3 stays the same brightness.

This page titled [5.6: Circuit Problem Solving](#) is shared under a [CC BY 4.0](#) license and was authored, remixed, and/or curated by [Dina Zhabinskaya](#).