

3.7: Characteristic Impedance

Characteristic impedance is the ratio of voltage to current for a wave that is propagating in single direction on a transmission line. This is an important parameter in the analysis and design of circuits and systems using transmission lines. In this section, we formally define this parameter and derive an expression for this parameter in terms of the equivalent circuit model introduced in Section 3.4.

Consider a transmission line aligned along the z axis. Employing some results from Section 3.6, recall that the phasor form of the wave equation in this case is

$$\frac{\partial^2}{\partial z^2} \tilde{V}(z) - \gamma^2 \tilde{V}(z) = 0 \quad (3.7.1)$$

where

$$\gamma \triangleq \sqrt{(R' + j\omega L')(G' + j\omega C')} \quad (3.7.2)$$

Equation 3.7.1 relates the potential phasor $\tilde{V}(z)$ to the equivalent circuit parameters R' , G' , C' , and L' . An equation of the same form relates the current phasor $\tilde{I}(z)$ to the equivalent circuit parameters:

$$\frac{\partial^2}{\partial z^2} \tilde{I}(z) - \gamma^2 \tilde{I}(z) = 0 \quad (3.7.3)$$

Since both $\tilde{V}(z)$ and $\tilde{I}(z)$ satisfy the *same* linear homogeneous differential equation, they may differ by no more than a multiplicative constant. Since $\tilde{V}(z)$ is potential and $\tilde{I}(z)$ is current, that constant can be expressed in units of impedance. Specifically, this is the *characteristic impedance*, so-named because it depends only on the materials and cross-sectional geometry of the transmission line – i.e., things which determine γ – and not length, excitation, termination, or position along the line.

To derive the characteristic impedance, first recall that the general solutions to Equations 3.7.1 and 3.7.3 are

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z} \quad (3.7.4)$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z} \quad (3.7.5)$$

where V_0^+ , V_0^- , I_0^+ , and I_0^- are complex-valued constants whose values are determined by boundary conditions; i.e., constraints on $\tilde{V}(z)$ and $\tilde{I}(z)$ at some position(s) along the line. Also, we will make use of the telegrapher's equations (Section 3.5):

$$-\frac{\partial}{\partial z} \tilde{V}(z) = [R' + j\omega L'] \tilde{I}(z) \quad (3.7.6)$$

$$-\frac{\partial}{\partial z} \tilde{I}(z) = [G' + j\omega C'] \tilde{V}(z) \quad (3.7.7)$$

We begin by differentiating Equation 3.7.4 with respect to z , which yields

$$\frac{\partial}{\partial z} \tilde{V}(z) = -\gamma [V_0^+ e^{-\gamma z} - V_0^- e^{+\gamma z}]$$

Now we use this to eliminate $\partial \tilde{V}(z)/\partial z$ in Equation 3.7.6, yielding

$$\gamma [V_0^+ e^{-\gamma z} - V_0^- e^{+\gamma z}] = [R' + j\omega L'] \tilde{I}(z)$$

Solving the above equation for $\tilde{I}(z)$ yields:

$$\tilde{I}(z) = \frac{\gamma}{R' + j\omega L'} [V_0^+ e^{-\gamma z} - V_0^- e^{+\gamma z}]$$

Comparing this to Equation 3.7.5, we note

$$I_0^+ = \frac{\gamma}{R' + j\omega L'} V_0^+$$

$$I_0^- = \frac{-\gamma}{R' + j\omega L'} V_0^-$$

We now make the substitution

$$Z_0 = \frac{R' + j\omega L'}{\gamma} \quad (3.7.8)$$

and observe

$$\frac{V_0^+}{I_0^+} = \frac{-V_0^-}{I_0^-} \triangleq Z_0$$

As anticipated, we have found that coefficients in the equations for potentials and currents are related by an impedance, namely, Z_0 . Characteristic impedance can be written entirely in terms of the equivalent circuit parameters by substituting Equation 3.7.2 into Equation 3.7.8, yielding:

$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

The characteristic impedance Z_0 (Ω) is the ratio of potential to current in a wave traveling in a single direction along the transmission line.

Take care to note that Z_0 is *not* the ratio of $\tilde{V}(z)$ to $\tilde{I}(z)$ in general; rather, Z_0 relates only the potential and current waves traveling in the *same* direction.

Finally, note that transmission lines are normally designed to have a characteristic impedance that is completely real-valued – that is, with no imaginary component. This is because the imaginary component of an impedance represents energy *storage* (think of capacitors and inductors), whereas the purpose of a transmission line is energy *transfer*.

This page titled 3.7: Characteristic Impedance is shared under a CC BY-SA 4.0 license and was authored, remixed, and/or curated by Steven W. Ellingson (Virginia Tech Libraries' Open Education Initiative) .

- **3.7: Characteristic Impedance** by Steven W. Ellingson is licensed CC BY-SA 4.0. Original source: <https://doi.org/10.21061/electromagnetics-vol-1>.