

CHAPTER OVERVIEW

3: Electromagnetic Fields in Simple Devices and Circuits

3.1: Resistors and Capacitors

3.2: Inductors and Transformers

3.3: Quasistatic Behavior of Devices

3.4: General circuits and solution methods

3.5: Two-element circuits and RLC resonators

This page titled [3: Electromagnetic Fields in Simple Devices and Circuits](#) is shared under a [CC BY-NC-SA 4.0](#) license and was authored, remixed, and/or curated by [David H. Staelin \(MIT OpenCourseWare\)](#) via [source content](#) that was edited to the style and standards of the LibreTexts platform.