

27.6: General Questions

1. Can you unscrew a bulb from a series circuit without affecting the flow of electrons?
2. Can you unscrew a bulb from a parallel circuit without affecting the flow of electrons?
3. How do you think most of the circuits in your home are wired, in series or in parallel? What evidence do you have?

Contributors and Attributions

- Template:ContribCCPhySc101L

27.6: General Questions is shared under a [CC BY](#) license and was authored, remixed, and/or curated by LibreTexts.