

## 27.5: Analysis

---

1. Compare and contrast series and parallel circuits, based on your observations.
2. Calculate the resistance for each of your 3 bulb circuits. Assume each bulb has 2 Ohms of resistance and neglect any resistance provided by the rest of the system.
3. How were you able to verify that you had both series connections and parallel connections in your combination circuit?

### Contributors and Attributions

- Template:ContribCCPhySc101L

---

27.5: Analysis is shared under a [CC BY](#) license and was authored, remixed, and/or curated by LibreTexts.