

## 6.S: Direct-Current Circuits (Summary)

### Key Terms

<b>ammeter</b>	instrument that measures current
<b>electromotive force (emf)</b>	energy produced per unit charge, drawn from a source that produces an electrical current
<b>equivalent resistance</b>	resistance of a combination of resistors; it can be thought of as the resistance of a single resistor that can replace a combination of resistors in a series and/or parallel circuit
<b>internal resistance</b>	amount of resistance to the flow of current within the voltage source
<b>junction rule</b>	sum of all currents entering a junction must equal the sum of all currents leaving the junction
<b>Kirchhoff's rules</b>	set of two rules governing current and changes in potential in an electric circuit
<b>loop rule</b>	algebraic sum of changes in potential around any closed circuit path (loop) must be zero
<b>potential difference</b>	difference in electric potential between two points in an electric circuit, measured in volts
<b>potential drop</b>	loss of electric potential energy as a current travels across a resistor, wire, or other component
<b>RC circuit</b>	circuit that contains both a resistor and a capacitor
<b>shock hazard</b>	hazard in which an electric current passes through a person
<b>terminal voltage</b>	potential difference measured across the terminals of a source when there is no load attached
<b>thermal hazard</b>	hazard in which an excessive electric current causes undesired thermal effects
<b>three-wire system</b>	wiring system used at present for safety reasons, with live, neutral, and ground wires
<b>voltmeter</b>	instrument that measures voltage

### Key Equations

Terminal voltage of a single voltage source	$V_{terminal} = \mathcal{E} - Ir_{eq}$
Equivalent resistance of a series circuit	$R_{eq} = R_1 + R_2 + R_3 + \cdots + R_{N-1} + R_N = \sum_{i=1}^N R_i$
Equivalent resistance of a parallel circuit	$R_{eq} = (\frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_N})^{-1} = (\sum_{i=1}^N \frac{1}{R_i})^{-1}$
Junction rule	$\sum I_{in} = \sum I_{out}$
Loop rule	$\sum V = 0$
Terminal voltage of N voltage sources in series	$V_{terminal} = \sum_{i=1}^N \mathcal{E}_i - I \sum_{i=1}^N r_i = \sum_{i=1}^N \mathcal{E}_i - Ir_{eq}$
Terminal voltage of N voltage sources in parallel	$V_{terminal} = \mathcal{E} - I \sum_{i=1}^N (\frac{1}{r_i})^{-1} = \mathcal{E} - Ir_{eq}$
Charge on a charging capacitor	$q(t) = C\mathcal{E}(1 - e^{-\frac{t}{RC}}) = Q(1 - e^{-\frac{t}{\tau}})$
Time constant	$\tau = RC$

Current during charging of a capacitor	$I = \frac{\varepsilon}{R} e^{-\frac{t}{RC}} = I_o e^{-\frac{t}{RC}}$
Charge on a discharging capacitor	$q(t) = Q e^{-\frac{t}{\tau}}$
Current during discharging of a capacitor	$I(t) = -\frac{Q}{RC} e^{-\frac{t}{\tau}}$

## Summary

### 10.2 Electromotive Force

- All voltage sources have two fundamental parts: a source of electrical energy that has a characteristic electromotive force (emf), and an internal resistance  $r$ . The emf is the work done per charge to keep the potential difference of a source constant. The emf is equal to the potential difference across the terminals when no current is flowing. The internal resistance  $r$  of a voltage source affects the output voltage when a current flows.
- The voltage output of a device is called its terminal voltage  $V_{terminal}$  and is given by  $V_{terminal} = \varepsilon - Ir$ , where  $I$  is the electric current and is positive when flowing away from the positive terminal of the voltage source and  $r$  is the internal resistance.

### 10.3 Resistors in Series and Parallel

- The equivalent resistance of an electrical circuit with resistors wired in a series is the sum of the individual resistances:

$$R_s = R_1 + R_2 + R_3 + \cdots = \sum_{i=1}^N R_i .$$

- Each resistor in a series circuit has the same amount of current flowing through it.
- The potential drop, or power dissipation, across each individual resistor in a series is different, and their combined total is the power source input.
- The equivalent resistance of an electrical circuit with resistors wired in parallel is less than the lowest resistance of any of the components and can be determined using the formula

$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \cdots \right)^{-1} = \left( \sum_{i=1}^N \frac{1}{R_i} \right)^{-1} .$$

- Each resistor in a parallel circuit has the same full voltage of the source applied to it.
- The current flowing through each resistor in a parallel circuit is different, depending on the resistance.
- If a more complex connection of resistors is a combination of series and parallel, it can be reduced to a single equivalent resistance by identifying its various parts as series or parallel, reducing each to its equivalent, and continuing until a single resistance is eventually reached.

### 10.4 Kirchhoff's Rules

- Kirchhoff's rules can be used to analyze any circuit, simple or complex. The simpler series and parallel connection rules are special cases of Kirchhoff's rules.
- Kirchhoff's first rule, also known as the junction rule, applies to the charge to a junction. Current is the flow of charge; thus, whatever charge flows into the junction must flow out.
- Kirchhoff's second rule, also known as the loop rule, states that the voltage drop around a loop is zero.
- When calculating potential and current using Kirchhoff's rules, a set of conventions must be followed for determining the correct signs of various terms.
- When multiple voltage sources are in series, their internal resistances add together and their emfs add together to get the total values.
- When multiple voltage sources are in parallel, their internal resistances combine to an equivalent resistance that is less than the individual resistance and provides a higher current than a single cell.
- Solar cells can be wired in series or parallel to provide increased voltage or current, respectively.

### 10.5 Electrical Measuring Instruments

- Voltmeters measure voltage, and ammeters measure current. Analog meters are based on the combination of a resistor and a galvanometer, a device that gives an analog reading of current or voltage. Digital meters are based on analog-to-digital converters and provide a discrete or digital measurement of the current or voltage.
- A voltmeter is placed in parallel with the voltage source to receive full voltage and must have a large resistance to limit its effect on the circuit.

- An ammeter is placed in series to get the full current flowing through a branch and must have a small resistance to limit its effect on the circuit.
- Standard voltmeters and ammeters alter the circuit they are connected to and are thus limited in accuracy.
- Ohmmeters are used to measure resistance. The component in which the resistance is to be measured should be isolated (removed) from the circuit.

### 10.6 RC Circuits

- An **RC** circuit is one that has both a resistor and a capacitor.
- The time constant  $\tau$  for an **RC** circuit is  $\tau = RC$ .
- When an initially uncharged ( $q = 0$  at  $t = 0$ ) capacitor in series with a resistor is charged by a dc voltage source, the capacitor asymptotically approaches the maximum charge.
- As the charge on the capacitor increases, the current exponentially decreases from the initial current:  $I_0 = \mathcal{E}/R$ .
- If a capacitor with an initial charge **Q** is discharged through a resistor starting at  $t = 0$ , then its charge decreases exponentially. The current flows in the opposite direction, compared to when it charges, and the magnitude of the charge decreases with time.

### 10.7 Household Wiring and Electrical Safety

- The two types of electric hazards are thermal (excessive power) and shock (current through a person). Electrical safety systems and devices are employed to prevent thermal and shock hazards.
- Shock severity is determined by current, path, duration, and ac frequency.
- Circuit breakers and fuses interrupt excessive currents to prevent thermal hazards.
- The three-wire system guards against thermal and shock hazards, utilizing live/hot, neutral, and ground wires, and grounding the neutral wire and case of the appliance.
- A ground fault circuit interrupter (GFCI) prevents shock by detecting the loss of current to unintentional paths.

### Contributors and Attributions

Samuel J. Ling (Truman State University), Jeff Sanny (Loyola Marymount University), and Bill Moebs with many contributing authors. This work is licensed by OpenStax University Physics under a [Creative Commons Attribution License \(by 4.0\)](#).

---

This page titled [6.S: Direct-Current Circuits \(Summary\)](#) is shared under a [CC BY](#) license and was authored, remixed, and/or curated by [OpenStax](#).

- [10.8: Direct-Current Circuits \(Summary\)](#) by [OpenStax](#) is licensed [CC BY 4.0](#). Original source: <https://openstax.org/details/books/university-physics-volume-2>.