

## 8.9: Capacitance (Answers)

### Check Your Understanding

8.1.  $1.1 \times 10^{-3} m$

8.3. 3.59 cm, 17.98 cm

8.4. a. 25.0 pF;

b. 9.2

8.5. a.  $C = 0.86 pF$ ,  $Q_1 = 10 pC$ ,  $Q_2 = 3.4 pC$ ,  $Q_3 = 6.8 pC$ ;

b.  $C = 2.3 pF$ ,  $Q_1 = 12 pC$ ,  $Q_2 = Q_3 = 16 pC$ ;

c.  $C = 2.3 pF$ ,  $Q_1 = 9.0 pC$ ,  $Q_2 = 18 pC$ ,  $Q_3 = 12 pC$ ,  $Q_4 = 15 pC$

8.6. a.  $4.0 \times 10^{-13} J$ ; b. 9 times

8.7. a. 3.0; b.  $C = 3.0 C_0$

8.9. a.  $C_0 = 20 pF$ ,  $C = 42 pF$ ;

b.  $Q_0 = 0.8 nC$ ,  $Q = 1.7 nC$ ;

c.  $V_0 = V = 40 V$ ; d.  $U_0 = 16 nJ$ ,  $U = 34 nJ$

### Conceptual Questions

1. no; yes

3. false

5. no

7.  $3.0 \mu F$ ,  $0.33 \mu F$

9. answers may vary

11. Dielectric strength is a critical value of an electrical field above which an insulator starts to conduct; a dielectric constant is the ratio of the electrical field in vacuum to the net electrical field in a material.

13. Water is a good solvent.

15. When energy of thermal motion is large (high temperature), an electrical field must be large too in order to keep electric dipoles aligned with it.

17. answers may vary

### Problems

19. 21.6 mC

21. 1.55 V

23. 25.0 nF

25.  $1.1 \times 10^{-3} m^2$

27. 500  $\mu C$

29. 1:16

31. a. 1.07 nC;

b. 267 V, 133 V

33.  $0.29 \mu F$

34. 500 capacitors; connected in parallel

35.  $3.08\mu F$  (series) and  $13.0\mu$  (parallel)

37.  $11.4\mu F$

39. 0.89 mC; 1.78 mC; 444 V

41.  $7.5\mu J$

43. a. 405 J; b. 90.0 mC

45. 1.15 J

47. a.  $4.43 \times 10^{-9} F$ ;

b. 0.453 V;

c.  $4.53 \times 10^{-10} J$ ;

d. no

49. 0.7 mJ

51. a. 7.1 pF;

b. 42 pF

53. a. before 3.00 V; after 0.600 V;

b. before 1500 V/m; after 300 V/m

55. a. 3.91;

b. 22.8 V

57. a. 37 nC;

b. 0.4 MV/m;

c. 19 nC

59. a.  $4.4\mu F$ ;

b.  $4.0 \times 10^{-5} C$

61.  $0.0135m^2$

63.  $0.185\mu J$

### Additional Problems

65. a. 0.277 nF;

b. 27.7 nC;

c. 50 kV/m

67. a. 0.065 F;


b. 23,000 C;

c. 4.0 GJ

69. a.  $75.6\mu C$ ; b. 10.8 V

71. a. 0.13 J;

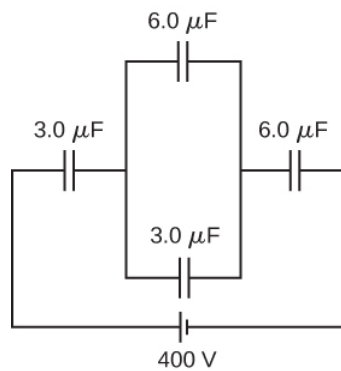b. no, because of resistive heating in connecting wires that is always present, but the circuit schematic does not indicate resistors



73. a.  $-3.00\mu F$ ;

b. You cannot have a negative  $C_2$  capacitance.

c. The assumption that they were hooked up in parallel, rather than in series, is incorrect. A parallel connection always produces a greater capacitance, while here a smaller capacitance was assumed. This could only happen if the capacitors are connected in series.

75. a. 14.2 kV;

b. The voltage is unreasonably large, more than 100 times the breakdown voltage of nylon.

c. The assumed charge is unreasonably large and cannot be stored in a capacitor of these dimensions.

### Challenge Problems

77. a. 89.6 pF;

b. 6.09 kV/m;

c. 4.47 kV/m;

d. no

79. a. 421 J;

b. 53.9 mF

81.  $C = \epsilon_0 A / (d_1 + d_2)$

83. proof

This page titled [8.9: Capacitance \(Answers\)](#) is shared under a [CC BY 4.0](#) license and was authored, remixed, and/or curated by [OpenStax](#) via [source content](#) that was edited to the style and standards of the LibreTexts platform.