

12.3: Electrical Analogue

Suppose that an alternating potential difference $E = \hat{E} \sin \omega t$ is applied across an LCR circuit. We refer to Equation 11.6.3, and we see that the equation that governs the charge on the capacitor is

$$L\ddot{Q} + R\dot{Q} + \frac{Q}{C} = \hat{E} \sin \omega t. \quad (12.3.1)$$

We can differentiate both sides with respect to time, and divide by L , and hence see that the current is given by

$$\ddot{I} + \frac{R}{L}\dot{I} + \frac{1}{LC}I = \frac{\hat{E}\omega}{L} \cos \omega t. \quad (12.3.2)$$

We can compare this directly with Equation 12.2.2, so that we have

$$\gamma = \frac{R}{L}, \quad \omega_0^2 = \frac{1}{LC}, \quad \hat{f} = \frac{\hat{E}\omega}{L}. \quad (12.3.3)$$

Then, by comparison with Equation 12.2.5, we see that I will lag behind E by α , where

$$\tan \alpha = \frac{\frac{R\omega}{L}}{\frac{1}{LC} - \omega^2} = \frac{R}{\frac{1}{C\omega} - L\omega}. \quad (12.3.4)$$

This is just what we obtain from the more familiar complex number approach to alternating current circuits.

This page titled [12.3: Electrical Analogue](#) is shared under a [CC BY-NC 4.0](#) license and was authored, remixed, and/or curated by [Jeremy Tatum](#) via [source content](#) that was edited to the style and standards of the LibreTexts platform.