

### 3.15: Input Impedance of a Terminated Lossless Transmission Line

Consider Figure 3.15.1, which shows a lossless transmission line being driven from the left and which is terminated by an impedance  $Z_L$  on the right. If  $Z_L$  is equal to the characteristic impedance  $Z_0$  of the transmission line, then the input impedance  $Z_{in}$  will be equal to  $Z_L$ . Otherwise  $Z_{in}$  depends on both  $Z_L$  and the characteristics of the transmission line. In this section, we determine a general expression for  $Z_{in}$  in terms of  $Z_L$ ,  $Z_0$ , the phase propagation constant  $\beta$ , and the length  $l$  of the line.

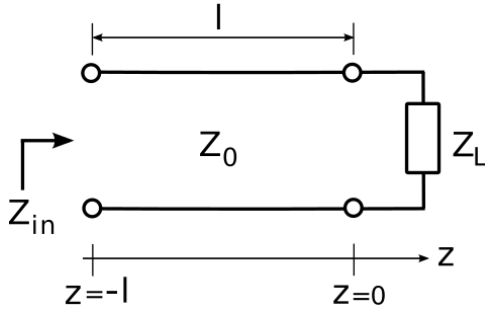


Figure 3.15.1 A transmission line driven by a source on the left and terminated by an impedance  $Z_L$  at  $z = 0$  on the right

Using the coordinate system indicated in Figure 3.15.1, the interface between source and transmission line is located at  $z = -l$ . Impedance is defined as the ratio of potential to current, so:

$$Z_{in}(l) \triangleq \frac{\tilde{V}(z = -l)}{\tilde{I}(z = -l)}$$

Now employing expressions for  $\tilde{V}(z)$  and  $\tilde{I}(z)$  from Section 3.13 with  $z = -l$ , we find:

$$\begin{aligned} Z_{in}(l) &= \frac{V_0^+ (e^{+j\beta l} + \Gamma e^{-j\beta l})}{V_0^+ (e^{+j\beta l} - \Gamma e^{-j\beta l}) / Z_0} \\ &= Z_0 \frac{e^{+j\beta l} + \Gamma e^{-j\beta l}}{e^{+j\beta l} - \Gamma e^{-j\beta l}} \end{aligned}$$

Multiplying both numerator and denominator by  $e^{-j\beta l}$ :

$$Z_{in}(l) = Z_0 \frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}} \quad (3.15.1)$$

Recall that  $\Gamma$  in the above expression is:

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (3.15.2)$$

Summarizing:

Equation 3.15.1 is the input impedance of a lossless transmission line having characteristic impedance  $Z_0$  and which is terminated into a load  $Z_L$ . The result also depends on the length and phase propagation constant of the line.

Note that  $Z_{in}(l)$  is periodic in  $l$ . Since the argument of the complex exponential factors is  $2\beta l$ , the frequency at which  $Z_{in}(l)$  varies is  $\beta/\pi$ , and since  $\beta = 2\pi/\lambda$ , the associated period is  $\lambda/2$ . This is very useful to keep in mind because it means that all possible values of  $Z_{in}(l)$  are achieved by varying  $l$  over  $\lambda/2$ . In other words, changing  $l$  by more than  $\lambda/2$  results in an impedance which could have been obtained by a smaller change in  $l$ . Summarizing to underscore this important idea:

The input impedance of a terminated lossless transmission line is periodic in the length of the transmission line, with period  $\lambda/2$ .

Not surprisingly,  $\lambda/2$  is also the period of the standing wave (Section 3.13). This is because – once again – the variation with length is due to the interference of incident and reflected waves.

Also worth noting is that Equation 3.15.1 can be written entirely in terms of  $Z_L$  and  $Z_0$ , since  $\Gamma$  depends only on these two parameters. Here's that version of the expression:

$$Z_{in}(l) = Z_0 \left[ \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right] \quad (3.15.3)$$

This expression can be derived by substituting Equation 3.15.2 into Equation 3.15.1 and is left as an exercise for the student.

Finally, note that the argument  $\beta l$  appearing Equations 3.15.1 and 3.15.3 has units of radians and is referred to as *electrical length*. Electrical length can be interpreted as physical length expressed with respect to wavelength and has the advantage that analysis can be made independent of frequency.

---

This page titled 3.15: Input Impedance of a Terminated Lossless Transmission Line is shared under a CC BY-SA 4.0 license and was authored, remixed, and/or curated by Steven W. Ellingson (Virginia Tech Libraries' Open Education Initiative).

- 3.15: Input Impedance of a Terminated Lossless Transmission Line by Steven W. Ellingson is licensed CC BY-SA 4.0. Original source: <https://doi.org/10.21061/electromagnetics-vol-1>.