

## 10.5: RL Circuits

### Learning Objectives

By the end of this section, you will be able to:

- Analyze circuits that have an inductor and resistor in series
- Describe how current and voltage exponentially grow or decay based on the initial conditions

A circuit with resistance and self-inductance is known as an **RL circuit**. Figure 10.5.1a shows an **RL circuit** consisting of a resistor, an inductor, a constant source of emf, and switches  $S_1$  and  $S_2$ . When  $S_1$  is closed, the circuit is equivalent to a single-loop circuit consisting of a resistor and an inductor connected across a source of emf (Figure 10.5.1b). When  $S_1$  is opened and  $S_2$  is closed, the circuit becomes a single-loop circuit with only a resistor and an inductor (Figure 10.5.1c).

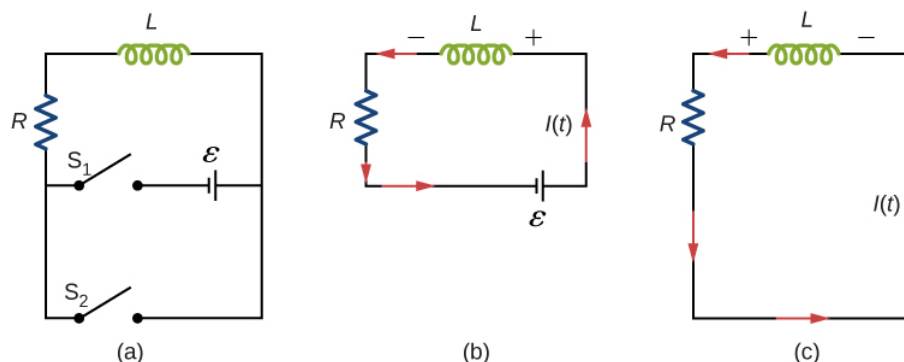


Figure 10.5.1: (a) An RL circuit with switches  $S_1$  and  $S_2$ . (b) The equivalent circuit with  $S_1$  closed and  $S_2$  open. (c) The equivalent circuit after  $S_1$  is opened and  $S_2$  is closed.

We first consider the **RL circuit** of Figure 10.5.1b. Once  $S_1$  is closed and  $S_2$  is open, the source of emf produces a current in the circuit. If there were no self-inductance in the circuit, the current would rise immediately to a steady value of  $\mathcal{E}/R$ . However, from Faraday's law, the increasing current produces an emf  $V_L = -L(dI/dt)$  across the inductor. In accordance with **Lenz's law**, the induced emf counteracts the increase in the current and is directed as shown in the figure. As a result,  $I(t)$  starts at zero and increases asymptotically to its final value.

Applying **Kirchhoff's loop rule** to this circuit, we obtain

$$\mathcal{E} - L \frac{dI}{dt} - IR = 0, \quad (10.5.1)$$

which is a first-order differential equation for  $I(t)$ . Notice its similarity to the equation for a capacitor and resistor in series (see **RC Circuits**). Similarly, the solution to Equation 10.5.1 can be found by making substitutions in the equations relating the capacitor to the inductor. This gives

$$I(t) = \frac{\mathcal{E}}{R}(1 - e^{-Rt/L}) \quad (10.5.2)$$

$$= \frac{\mathcal{E}}{R}(1 - e^{-t/\tau_L}), \quad (10.5.3)$$

where

$$\tau_L = L/R \quad (10.5.4)$$

is the **inductive time constant** of the circuit.

The current  $I(t)$  is plotted in Figure 10.5.2a. It starts at zero, and as  $t \rightarrow \infty$ ,  $I(t)$  approaches  $\mathcal{E}/R$  asymptotically. The induced emf  $V_L(t)$  is directly proportional to  $dI/dt$ , or the slope of the curve. Hence, while at its greatest immediately after the switches are thrown, the induced emf decreases to zero with time as the current approaches its final value of  $\mathcal{E}/R$ . The circuit then becomes equivalent to a resistor connected across a source of emf.

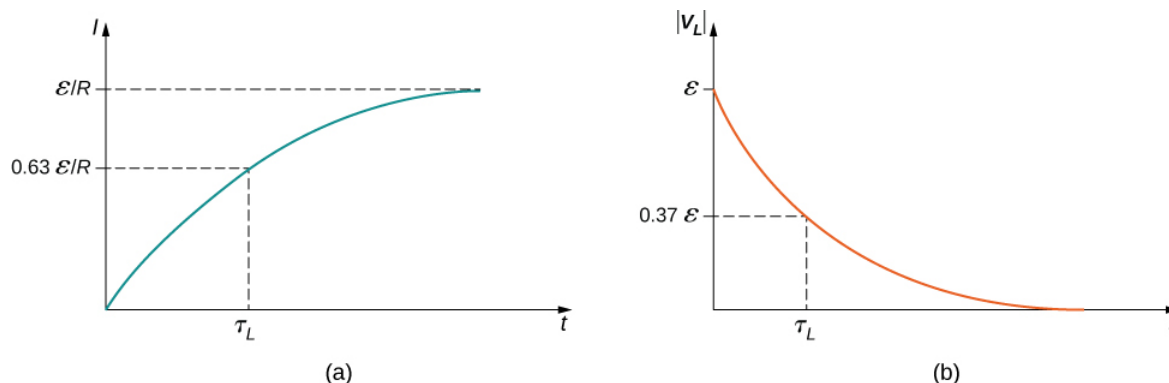


Figure 10.5.2: Time variation of (a) the electric current and (b) the magnitude of the induced voltage across the coil in the circuit of Figure 10.5.1b.

The energy stored in the magnetic field of an inductor is

$$U_L = \frac{1}{2} LI^2.$$

Thus, as the current approaches the maximum current  $\mathcal{E}/R$ , the stored energy in the inductor increases from zero and asymptotically approaches a maximum of  $L(\mathcal{E}/R)^2/2$ .

The time constant  $\tau_L$  tells us how rapidly the current increases to its final value. At  $t = \tau_L$ , the current in the circuit is, from Equation 10.5.3,

$$I(\tau_L) = \frac{\mathcal{E}}{R}(1 - e^{-1}) = 0.63 \frac{\mathcal{E}}{R},$$

which is 63% of the final  $\mathcal{E}/R$ . The smaller the inductive time constant  $\tau_L = L/R$ , the more rapidly the current approaches  $\mathcal{E}/R$ .

We can find the time dependence of the induced voltage across the inductor in this circuit by using  $V_L(t) = -L(dI/dt)$  and Equation 10.5.3

$$V_L(t) = -L \frac{dI}{dt} = -\mathcal{E}e^{-t/\tau_L}.$$

The magnitude of this function is plotted in Figure 10.5.2b. The greatest value of  $L(dI/dt)$  is  $\mathcal{E}$ ; it occurs when  $dI/dt$  is greatest, which is immediately after  $S_1$  is closed and  $S_2$  is opened. In the approach to steady state,  $dI/dt$  decreases to zero. As a result, the voltage across the inductor also vanishes as  $t \rightarrow \infty$ .

The time constant  $\tau_L$  also tells us how quickly the induced voltage decays. At  $t = \tau_L$  the magnitude of the induced voltage is

$$|V_L(\tau_L)| = \mathcal{E}e^{-1} = 0.37\mathcal{E} = 0.37V(0).$$

The voltage across the inductor therefore drops to about 37% of its initial value after one time constant. The shorter the time constant  $\tau_L$ , the more rapidly the voltage decreases.

After enough time has elapsed so that the current has essentially reached its final value, the positions of the switches in Figure 10.5.1a are reversed, giving us the circuit in part (c). At  $t = 0$ , the current in the circuit is  $I(0) = \mathcal{E}/R$ . With Kirchhoff's loop rule, we obtain

$$IR + L \frac{dI}{dt} = 0.$$

The solution to this equation is similar to the solution of the equation for a discharging capacitor, with similar substitutions. The current at time  $t$  is then

$$I(t) = \frac{\mathcal{E}}{R}e^{-t/\tau_L}.$$

The current starts at  $I(0) = \mathcal{E}/R$  and decreases with time as the energy stored in the inductor is depleted (Figure 10.5.3).

The time dependence of the voltage across the inductor can be determined from  $V_L = -L(dI/dt)$ :

$$V_L(0) = \epsilon e^{-t/\tau_L}. \quad (10.5.5)$$

This voltage is initially  $V_L(0) = \epsilon$ , and it decays to zero like the current. The energy stored in the magnetic field of the inductor,  $LI^2/2$ , also decreases exponentially with time, as it is dissipated by Joule heating in the resistance of the circuit.

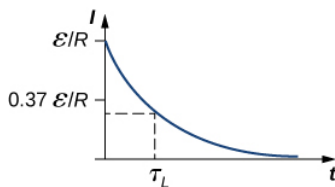


Figure 10.5.3: Time variation of electric current in the RL circuit of Figure 10.5.1c. The induced voltage across the coil also decays exponentially.

### ✓ Example 10.5.1: An RL Circuit with a Source of emf

In the circuit of Figure 10.5.1a, let  $\epsilon = 2.0 \text{ V}$ ,  $R = 4.0 \Omega$ , and  $L = 4.0 \text{ H}$ . With  $S_1$  closed and  $S_2$  open (Figure 10.5.1b), (a) what is the time constant of the circuit? (b) What are the current in the circuit and the magnitude of the induced emf across the inductor at  $t = 0$ , at  $t = 2.0\tau_L$ , and as  $t \rightarrow \infty$ ?

#### Strategy

The time constant for an inductor and resistor in a series circuit is calculated using Equation 10.5.4. The current through and voltage across the inductor are calculated by the scenarios detailed from Equation 10.5.3 and Equation 10.5.5.

#### Solution

1. The inductive time constant is

$$\tau_L = \frac{L}{R} = \frac{4.0 \text{ H}}{4.0 \Omega} = 1.0 \text{ s}.$$

2. The current in the circuit of Figure 10.5.1b increases according to Equation 10.5.3

$$I(t) = \frac{\epsilon}{R}(1 - e^{-t/\tau_L}).$$

At  $t = 0$ ,

$$(1 - e^{-t/\tau_L}) = (1 - 1) = 0; \text{ so } I(0) = 0.$$

At  $t = 2.0\tau_L$  and  $t \rightarrow \infty$ , we have, respectively,

$$I(2.0\tau_L) = \frac{\epsilon}{R}(1 - e^{-2.0}) = (0.50 \text{ A})(0.86) = 0.43 \text{ A}$$

and

$$I(\infty) = \frac{\epsilon}{R} = 0.50 \text{ A}.$$

From Equation 10.5.5, the magnitude of the induced emf decays as

$$|V_L(t)| = \epsilon e^{-t/\tau_L}.$$

At  $t = 0$ ,  $t = 2.0\tau_L$ , and as  $t \rightarrow \infty$ , we obtain

$$|V_L(0)| = \epsilon = V,$$

$$|V_L(2.0\tau_L)| = (2.0 \text{ V})e^{-2.0} = 0.27 \text{ V}$$

and

$$|V_L(\infty)| = 0.$$

#### Significance

If the time of the measurement were much larger than the time constant, we would not see the decay or growth of the voltage across the inductor or resistor. The circuit would quickly reach the asymptotic values for both of these (Figure 10.5.4).

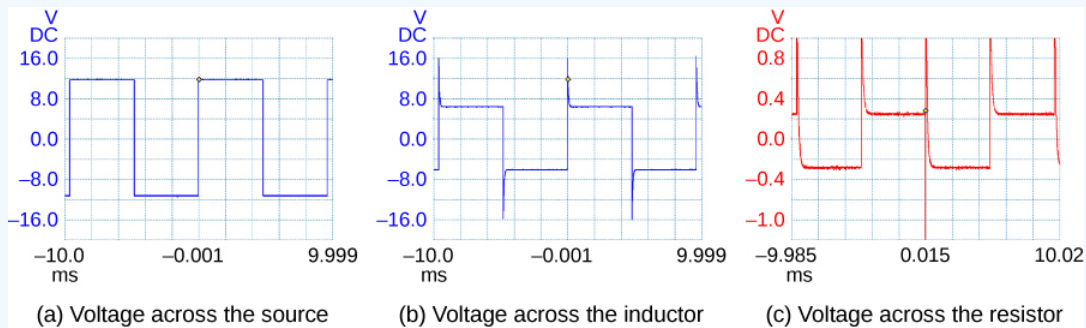


Figure 10.5.4: A generator in an **RL** circuit produces a square-pulse output in which the voltage oscillates between zero and some set value. These oscilloscope traces show (a) the voltage across the source; (b) the voltage across the inductor; (c) the voltage across the resistor.

### ✓ Example 10.5.1: An RL Circuit without a Source of emf

After the current in the **RL** circuit of Example 10.5.1 has reached its final value, the positions of the switches are reversed so that the circuit becomes the one shown in Figure 10.5.1c

- How long does it take the current to drop to half its initial value?
- How long does it take before the energy stored in the inductor is reduced to 1.0% of its maximum value?

#### Strategy

The current in the inductor will now decrease as the resistor dissipates this energy. Therefore, the current falls as an exponential decay. We can also use that same relationship as a substitution for the energy in an inductor formula to find how the energy decreases at different time intervals.

#### Solution

- With the switches reversed, the current decreases according to

$$I(t) = \frac{\epsilon}{R} e^{-t/\tau_L} = I(0) e^{-t/\tau_L}.$$

At a time **t** when the current is one-half its initial value, we have

$$I(t) = 0.50I(0) \text{ so } e^{-t/\tau_L} = 0.50,$$

and

$$t = -[\ln(0.50)]\tau_L = 0.69(1.0 \text{ s}) = 0.69 \text{ s}$$

where we have used the inductive time constant found in Example 10.5.1

- The energy stored in the inductor is given by

$$U_L(t) = \frac{1}{2} L [I(t)]^2 = \frac{1}{2} L \left( \frac{\epsilon}{R} e^{-t/\tau_L} \right)^2 = \frac{L\epsilon^2}{2R^2} e^{-2t/\tau_L}.$$

If the energy drops to 1.0% of its initial value at a time **t**, we have

$$U_L(t) = (0.010)U_L(0) \text{ or } \frac{L\epsilon^2}{2R^2} e^{-2t/\tau_L} = (0.010) \frac{L\epsilon^2}{2R^2}.$$

Upon canceling terms and taking the natural logarithm of both sides, we obtain

$$-\frac{2t}{\tau_L} = \ln(0.010),$$

so

$$t = -\frac{1}{2}\tau_L \ln(0.010).$$

Since  $\tau_L = 1.0 \text{ s}$ , the time it takes for the energy stored in the inductor to decrease to 1.0% of its initial value is

$$t = -\frac{1}{2}(1.0 \text{ s}) \ln(0.010) = 2.3 \text{ s}.$$

### Significance

This calculation only works if the circuit is at maximum current in situation (b) prior to this new situation. Otherwise, we start with a lower initial current, which will decay by the same relationship.

#### ? Exercise 10.5.1

Verify that **RC** and **L/R** have the dimensions of time

#### ? Exercise 10.5.2

- If the current in the circuit of in Figure 10.5.1b increases to 90% of its final value after 5.0 s, what is the inductive time constant?
- If  $R = 20 \Omega$ , what is the value of the self-inductance?
- If the  $R = 20 \Omega$  resistor is replaced with a  $R = 100 \Omega$  resistor, what is the time taken for the current to reach 90% of its final value?

### Answer

- a. 2.2 s; b. 43 H; c. 1.0 s

#### ? Exercise 10.5.3

For the circuit of in Figure 10.5.1b show that when steady state is reached, the difference in the total energies produced by the battery and dissipated in the resistor is equal to the energy stored in the magnetic field of the coil

This page titled [10.5: RL Circuits](#) is shared under a [CC BY 4.0](#) license and was authored, remixed, and/or curated by [OpenStax](#) via [source content](#) that was edited to the style and standards of the LibreTexts platform.

- 14.5: RL Circuits** by OpenStax is licensed [CC BY 4.0](#). Original source: <https://openstax.org/details/books/university-physics-volume-2>.