

CHAPTER OVERVIEW

6: Direct-Current (DC) Resistor Circuits

- [6.1: Introduction](#)
- [6.2: Source Voltage](#)
- [6.3: Resistors in Series and Parallel](#)
- [6.4: Kirchhoff's Rules and Resistor Circuits](#)
- [6.5: Application - Electrical Meters](#)
- [6.6: Application - Grounding and Electrical Safety](#)
- [6.7: Direct-Current Circuits \(Summary\)](#)
- [6.8: Direct-Current Circuits \(Exercise\)](#)
- [6.9: Direct-Current Circuits \(Answers\)](#)

6: Direct-Current (DC) Resistor Circuits is shared under a [not declared](#) license and was authored, remixed, and/or curated by LibreTexts.